

CONTENTS

Preface

1. Introduction	
1.1 Modulation – Demodulation	
1.2 $\Delta\Sigma$ Modulation	
1.3 Design and Implementation of $\Delta\Sigma$ Modulators	
1.4 Applications	
1.5 Book Organization	
2. Analog-to-Digital Conversion	
2.1 Introduction	
2.2 The Basic Concept of A/D Conversion	
2.3 Uniform Sampling	
2.4 Quantization Error and the Linear Model	
2.5 Sampling of Band-Pass Signals	
2.6 Oversampling Principles	
2.7 The Delta Modulator	
2.8 Performance of the Delta Modulator	
2.9 The Exponential DM	
2.10 The Concept of Noise Shaping	
2.11 Summary	
Problems	
References	
3. $\Delta\Sigma$ Modulators-Architectures	
3.1 Introduction	
3.2 First-Order $\Delta\Sigma$ Modulator	
3.2.1 Input and output waveforms	
3.2.2 SNR and PSD diagrams	
3.3 Comparison of the Delta and the $\Delta\Sigma$ Modulator.	
3.3.1 Linear DM	
3.3.2 Exponential DM	
3.3.3 $\Delta\Sigma$ Modulator	
3.4 Second-Order $\Delta\Sigma$ Modulators	
3.5 High-Order $\Delta\Sigma$ Modulators.	
3.6 Stability of Single-Stage $\Delta\Sigma$ Modulators	
3.7 Multi-Stage $\Delta\Sigma$ Modulators	
3.8 Multi-Bit $\Delta\Sigma$ Modulators.	
3.9 Hybrid $\Delta\Sigma$ Modulators	
3.10 Adaptive $\Delta\Sigma$ Modulators	
3.11 Band-Pass $\Delta\Sigma$ Modulators	
3.12 Summary	
Problems	
References	
4. Single-Bit Single-Stage $\Delta\Sigma$ Modulators, Modeling and Design	
4.1 Introduction.	
4.2 Modeling of $\Delta\Sigma$ Modulators	
4.2.1 Linear model	
4.2.2 Quasi-Linear model	
4.3 NTF Characteristics	

4.4	Stability of $\Delta\Sigma$ Modulators	
4.5	Stability Criteria	
4.6	Noise Transfer Function Determination.	
4.6.1	Optimizing the position of zeros	
4.6.2	Optimizing the position of poles	
4.7	$\Delta\Sigma$ Modulator Assessment	
4.8	Summary-Conclusions	
	Problems	
	References	
5.	Implementation of $\Delta\Sigma$ Modulators	
5.1	Introduction	
5.2	Basic Blocks of a $\Delta\Sigma$ Modulator for Analog-to-Digital Conversion	
	.	
5.2.1	The loop filter	
5.2.2	ADC and DAC.	
5.3	Continuous-Time Loop Filter implementation	
5.4	Circuit Design of a 1 st -Order $\Delta\Sigma$ Modulator	
5.5	Circuit Design of a 2 nd -Order $\Delta\Sigma$ Modulator	
5.6	Circuit Design of a 3 rd -Order $\Delta\Sigma$ Modulator	
5.7	Circuit Design of a 4 th -Order Band-pass $\Delta\Sigma$ Modulator	
5.8	Testing the Operation of $\Delta\Sigma$ Modulators Experimentally	
5.9	Low-Power, Low-Voltage $\Delta\Sigma$ Modulators	
5.10	Comments and Conclusions	
	Problems	
	References	
	Appendix: Z Transforms of Common Sequences	
6.	Practical Limitations of $\Delta\Sigma$ Modulators	
6.1	Introduction	
6.2	Practical Circuit Limitations	
6.2.1	Noise sources in the $\Delta\Sigma$ loop	
6.3	Effect of Thermal Noise	
6.3.1	SC circuits	
6.3.2	CT active RC circuits	
6.4	Effects of the Opamp non-Idealities.	
6.4.1	Thermal and flicker noise and DC offset of the opamp	
6.4.2	Finite opamp gain	
6.4.3	Finite bandwidth and slew-rate of the opamp	
	.	
6.5	Effect of Jitter	
6.5.1	SC circuits	
6.5.2	CT active RC circuits	
6.6	The Effect of Rise and Fall Times of DAC Pulses in CT Circuits	
6.7	A Comparison of SC and CT active RC Circuits	
6.8	DAC Errors	
6.9	Summary	
	Problems	

References	
7. Stabilization and Suppression of Tones for the Higher-Order Single-Stage $\Delta\Sigma$ Modulators	
7.1 Introduction	
7.2 Bounds of the Quantizer Input Using the Variable Gain Method	
7.3 Stabilization Methods	
7.3.1 Resetting the integrators	
7.3.2 Clipping the integrators	
7.3.3 Activation of local feedback loops around the integrators	
7.3.4 Reducing the order of the loop filter	
7.4 Comparison of the stabilization methods	
7.5 Tones in $\Delta\Sigma$ Modulators	
7.6 Fixed Techniques.	
7.6.1 Dithering	
7.6.2 Chaotic $\Delta\Sigma$ modulators	
7.6.3 Bit-flipping	
7.6.4 Comparison of fixed techniques	
7.7 Adaptive Techniques	
7.7.1 Adaptive dithering	
7.7.2 Adaptive bit-flipping	
7.7.3 Comparison of the adaptive techniques	
7.8 Summary	
References	
8. Decimation, Interpolation and Converters	
8.1 Introduction	
8.2 Rate Conversion	
8.2.1 Decimation	
8.2.2 Interpolation	
8.2.3 Decimation and interpolation filters	
8.2.4 Multi-stage rate conversion	
8.2.5 Comb filters	
8.2.6 Fractional rate conversion	
8.3 $\Delta\Sigma$ Modulators for ADC	
8.4 $\Delta\Sigma$ Modulators for DAC	
8.5 Summary.	
References	
9. Applications	
9.1 Introduction	
9.2 $\Delta\Sigma$ Modulation in Digital Radio	
9.2.1 Conversion bandwidth and resolution	
9.2.2 Sampling rate	
9.3 Frequency Synthesis	
9.3.1 Principles of the PLL operation	
9.3.2 $\Delta\Sigma$ Modulation in frequency synthesis	
9.4 Clock Generators Using $\Delta\Sigma$ Modulation	
9.5 $\Delta\Sigma$ Modulation in Analog-Input Digital Phase-Locked	

Loops for Frequency and Phase Demodulation	
. . .	
9.6 $\Delta\Sigma$ Modulation in Analog Oscillators	
9.7 Summary	
References	

Index